

# PAST EXAM PAPERS & MEMOS FOR ENGINEERING STUDIES N1-N6

THANK YOU FOR DOWNLOADING THE PAST EXAM PAPER, WE HOPE IT WILL BE OF HELP TO YOU. AT THE MOMENT WE **DO NOT HAVE MEMO FOR THE PAPER** BUT KEEP CHECKING OUT WEBSITE AND ONCE AVAILABLE WE WILL ADD IT FOR YOU.

## ARE YOU IN NEED OF MORE PAPERS

You might be in need of **more question papers** and answers (memos) as you prepare for your final exams. We have a FULL SINGLE DOWNLOAD in pdf of papers between **2014-2019**. **ALL THE PAPERS HAVE ANSWERS (MEMOS)**. We sell these at a **very discounted price** of **R299.00** per subject. Visit our website <https://previouspapers.co.za/shop/> to purchase a full download. Once you purchase, you get instant download and access. The online payment is also safe and we use [payfast](#) as it is used by all the banks in South Africa.

## PRICE OF THE PAPERS AT A BIG DISCOUNT

Previous papers are very important in ensuring you pass your final exams. The **actual value** of the papers access is way more than **R1 000** but we are making you access these for a small fee of **R299.00**. The small fee helps to maintain the website.

## BONUS PAPERS

We are also **adding bonus papers for free** which are papers between 2008-2011. These papers are very valuable as examiners usually repeat questions from old papers time and again. You get access to bonus papers after purchasing your paper.

## MORE FREE PAPERS

[Click here](#) to access more **FREE PAPERS**.



# higher education & training

---

Department:  
Higher Education and Training  
**REPUBLIC OF SOUTH AFRICA**

## **NATIONAL CERTIFICATE ELECTROTECHNOLOGY N3**

(11040343)

**16 April 2020 (X-paper)  
09:00–12:00**

**This question paper consists of 6 pages and one formula sheet of 3 pages.**

278Q1A2016



**DEPARTMENT OF HIGHER EDUCATION AND TRAINING**  
**REPUBLIC OF SOUTH AFRICA**  
NATIONAL CERTIFICATE  
ELECTROTECHNOLOGY N3  
TIME: 3 HOURS  
MARKS: 100

---


**INSTRUCTIONS AND INFORMATION**

1. Answer all the questions.
  2. Read all the questions carefully.
  3. Number the answers according to the numbering system used in this question paper.
  4. Start each question on a new page.
  5. Use only a black or blue pen.
  6. Write neatly and legibly.
-


**QUESTION 1**

- 1.1 Why are the field poles and the armature cores of DC machines laminated? (2)
- 1.2 Friction losses occur in the bearings that support the rotating armature.  
Name TWO types of bearings commonly used in DC machines.  (2)
- 1.3 State the function of each of the following components that make up the field system of a DC machine:
- 1.3.1 Field coils
- 1.3.2 Pole shoes (2 × 2) (4)
- 1.4 Choose the correct word(s) from those given in brackets. Write only the word (s) next to the question number (1.4.1–1.4.2) in the ANSWER BOOK.
- 1.4.1 (Wave-wound, Lap-wound, Armature winding) is for heavy- current machines  (2)
- 1.4.2 When the ampere-turns of the two windings oppose each other, the machine is said to be (cumulatively compounded, compound connected, differentially compounded). (2 × 1) (2)
- [10]**


**QUESTION 2**

- 2.1 State Faraday's first law of electromagnetic induction. (2)
- 2.2 Name TWO methods used to improve commutation and to reduce sparking. (2)
- 2.3 A 200 V DC, shunt-wound generator produces an armature current of 42,75 A. The resistance of the shunt field and armature are 125  $\Omega$  and 0,15  $\Omega$  respectively.  
Calculate the following:
- 2.3.1 Magnitude of the generated EMF  (2)
- 2.3.2 Efficiency of the generator if it is driven by a prime-mover rated at 9,5 kW (4)
- [10]**

**QUESTION 3**

- 3.1 Briefly explain the term *armature reaction* as applicable to DC machines. (2)
- 3.2 A 400 V, 15 kW, six-pole DC shunt motor has a lap-wound armature. The armature has 100 slots and there are four conductors per slot. The motor operates at a full-load efficiency of 85%. 
- Calculate the useful flux per pole if the motor develops a full-load torque of 136 Nm. Take the resistance of the field circuit to be 275  $\Omega$ . (5)
- 3.3 Draw the characteristic curve of a shunt motor showing torque against armature current. (3)
- [10]**

**QUESTION 4**

- 4.1 Name TWO places in a DC machine where iron losses occur. (2)
- 4.2 An overload relay is a protective device used to guard a motor against the harmful effects of an overload.
- Make a neat, fully labelled sketch of a simple thermal-type overload relay. Show and label the following parts in the relay:
- Contacts  
Bimetal strip   
Heating element (4)


- 4.3 During a brake test on a DC motor the following information was recorded:

Effective load on the brake drum	=	310 N
Pulley diameter	=	250 mm
Speed of shaft	=	875 r/min
Current drawn from the supply	=	17,5 A
Terminal voltage	=	220 V

Determine the efficiency of the motor.

(4)  
**[10]**

**QUESTION 5**

- 5.1 State what is meant by the following terms with regards to a sinusoidal waveform:
- 5.1.1 Cycle 
- 5.1.2 Frequency
- (2 × 2) (4)

5.2 An alternating current is represented by the following equation:

$$i = 13,5 \sin (376,991t)$$

Determine the following:

5.2.1 Frequency of this current



5.2.2 Average value of this current

5.2.3 Instantaneous value of the current, 0,75 milliseconds after the commencement of a cycle

(3 × 2)

(6)  
[10]

### QUESTION 6

A parallel circuit is supplied by a 90 V, 50 Hz voltage source. This parallel circuit comprises of a 40 Ω resistor, a 120 mH inductor and a 220 μF capacitor.

Calculate the following:

6.1 Current drawn by each component

(5)

6.2 Total current flowing through the circuit

(2)

6.3 Power factor of the circuit



(1)

6.4 Reactive power of the circuit

(2)

[10]

### QUESTION 7

7.1 An alternating current circuit has three powers associated with it. Copy the following table into your ANSWER BOOK and fill in the blank spaces.

SYMBOL	QUANTITY	FORMULA	UNIT
	True power	$VI \cos \phi$	
	Apparent power	$VI$	
	Reactive power	$VI \sin \phi$	

(6)

7.2 Draw a neat, fully labelled circuit diagram to show how the windings of a three-phase induction motor are connected in delta and then to the supply.

(3)

7.3 A large induction motor is started by means of a star-delta starter.



Determine the voltage across the stator windings of this 525 V induction motor while running at full-load speed.

(1)

**QUESTION 8**

- 8.1 The losses occurring in a transformer can be classified as either constant or variable losses.

Name TWO types of constant losses that occur in a transformer.



(2)

- 8.2 A three-phase distribution transformer has 800 turns on the primary side and 200 turns on the secondary side. For a primary voltage of 11 kV, calculate the secondary line voltage on open circuit if the transformer is connected in:

8.2.1 Delta-star

8.2.2 Star-delta

(2 × 4)

(8)  
[10]**QUESTION 9**

- 9.1 A moving-coil instrument gives a full-scale deflection if 20 mA flows through it. The internal resistance of coil is 85 Ω.

Determine the following:

9.1.1 The resistance required to use the instrument as an ammeter for a 6,2 A current flow.

(3)

9.1.2 The series resistance required to use it as a voltmeter up to 150 V.

(3)

- 9.2 Give the value of the following measuring instruments:

9.2.1 The usual full-scale deflection of an ammeter connected to a current transformer.

(1)



9.2.2 Output voltage of a potential transformer.

(1)

- 9.3 Name TWO mechanisms which are found in measuring instruments.

(2)

[10]

**QUESTION 10**

- 10.1 Draw a fully labelled IEC symbol for a silicon-controlled rectifier (SCR). (4)

- 10.2 Determine the number of inputs required so that the gate can produce 16 outputs. (2)



- 10.3 Convert  $15,8125_{10}$  into its binary equivalent. (4)

[10]

**TOTAL: 100**

**ELECTROTECHNOLOGY N3****FORMULA SHEET**

Any applicable formula may also be used.

$$1. E = V - I_a R_a$$

$$2. E = V + I_a R_a$$

$$3. E = 2p\Phi \frac{ZN}{60c}$$

$$4. N = \frac{V}{K\Phi}$$

$$5. T = \frac{0,318I_a Zp\Phi}{C}$$

$$6. \text{Efficiency} = \frac{VI}{VI + I_a^2 R_a + I_s V + C} \times 100\%$$

$$7. \text{Efficiency} = \frac{VI - (I_a^2 R_a + I_s V + C)}{VI} \times 100\%$$

$$8. \text{Efficiency} = \frac{2\pi N(W - S)r}{60VI} \times 100\%$$

$$9. \text{Efficiency} = \sqrt{\frac{I_1}{I_1 + I_2}} \times 100\%$$

$$10. E = Blv$$

$$11. e = E_m \sin 2\pi ft$$

$$12. i = I_m \sin 2\pi ft$$

$$13. e_{ave/gem} \text{ or } i_{ave/gem} = 0,637 E_m \text{ or } I_m$$

$$14. e_{rms/wgk} \text{ or } i_{rms/wgk} = 0,707 E_m \text{ or } I_m$$

$$15. E_{ave/gem} = \frac{e_1 + e_2 + e_3 + e_4 + \dots + e_n}{n} \quad \text{OR} \quad I_{ave/gem} = \frac{i_1 + i_2 + i_3 + \dots + i_n}{n}$$



$$16. E_{rms/wgk} = \sqrt{\frac{e_1^2 + e_2^2 + e_3^2 + \dots + e_n^2}{n}} \quad \text{OR} \quad I_{rms/wgk} = \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}}$$

$$17. \text{Form factor} = \frac{E_{rms/wgk}}{E_{ave/gem}} \quad \text{OR} \quad \frac{I_{RMS/WGK}}{i_{AVE/GEM}}$$

$$18. \text{Crest factor} = \frac{E_m}{E_{rms/wgk}} \quad \text{OR} \quad \frac{I_m}{I_{rms/wgk}}$$

$$19. I = \frac{V}{R}$$

$$20. X_L = 2\pi fL; \quad I = \frac{V}{X_L}$$

$$21. X_C = \frac{1}{2\pi fC}; \quad I = \frac{V}{X_C}$$

$$22. Z = \sqrt{R^2 + X_L^2}; \quad Z = \sqrt{R^2 + X_C^2}; \quad I = \frac{V}{Z}$$

$$23. \text{Tan } \theta = \frac{X_L}{R}; \quad \text{Tan } \theta = \frac{X_C}{R}$$

$$24. V_R = I \times R; \quad V_L = I \times X_L; \quad V_C = I \times X_C$$

$$25. Z = \sqrt{R^2 + (X_L - X_C)^2}; \quad Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$26. \text{Tan } \theta = \frac{X_L - X_C}{R}; \quad \text{Tan } \theta = \frac{X_C - X_L}{R}$$

$$27. P = V \times I; \quad P = I^2 R; \quad P = \frac{V^2}{R}$$

$$28. P = VI \cos \theta$$

$$29. \cos \theta = \frac{R}{Z}; \quad \cos \theta = \frac{W \text{ or } kW}{VA \text{ or } kVA}$$

$$30. I_{active} = I \cos \theta; \quad I_{reactive} = I \sin \theta$$

$$31. P = VI \cos \theta$$

$$Q = VI \sin \theta$$

$$32. f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$33. I = \sqrt{I_R^2 + I_L^2}; \quad \tan \theta = \frac{I_L}{I_R}$$

$$34. I = \sqrt{I_R^2 + I_C^2}; \quad \tan \theta = \frac{I_C}{I_R}$$

$$35. I = \sqrt{I_R^2 + (I_L - I_C)^2}; \quad \tan \theta = \frac{I_L - I_C}{I_R}$$

$$36. I = \sqrt{I_R^2 + (I_C - I_L)^2}; \quad \tan \theta = \frac{I_C - I_L}{I_R}$$

$$37. \cos \theta = \frac{I_R}{I}$$

$$38. V_L = V_p; \quad I_L = \sqrt{3}I_p$$

$$39. V_L = \sqrt{3}V_p; \quad I_L = I_p$$

$$40. W = \sqrt{3}V_L I_L \cos \theta \times \eta$$

$$41. \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$42. \text{kVA} = \frac{\sqrt{3}V_L I_L}{1000}$$

$$43. V_{shunt} = V_{meter}; \quad I_s R_s = I_m R_m$$

$$44. I_T = I_m + I_s$$

$$45. I_t = \frac{V_t}{R_t}$$